



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Lecture 12: VERILOG DESCRIPTION STYLES

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Description Styles in Verilog

- Two different styles of description:
 1. Data Flow
 - Continuous assignment *Using assignment statements.*
 2. Behavioral
 - Procedural assignment *Using procedural statements similar to a program in high-level language.*
 - Blocking
 - Non-blocking



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

2

Data Flow Style: Continuous Assignment

- Identified by the keyword “assign”.
- Forms a static binding between:
 - The “net” being assigned on the left-hand side (LHS).
 - The expression on the right-hand side (RHS), which may consist of both “net” and “register” type variables.
- The assignment is continuously active:
 - Almost exclusively used to model combinational circuits.
 - We shall also see some examples of modeling sequential circuit elements.

```
assign a = b + c;  
assign sign = Z[15];
```



- Some points to note:
 - A Verilog module can contain any number of “assign” statements.
 - Typically, the “assign” statements are followed by procedural descriptions.
 - The “assign” statements are used to model behavioral descriptions.
- We shall illustrate various usages of “assign” statements for modeling combinational and also some sequential logic blocks.



```
module generate_MUX (data, select, out);  
    input [15:0] data;  
    input [3:0] select;  
    output out;  
  
    assign out = data[select];  
endmodule
```

Non-constant index in
expression on RHS
generates a MUX



- Point to note:
 - Whenever there is an array reference on the RHS with a variable index, a MUX is generated by the synthesis tool.
 - If the index is a constant, just a wire will be generated.
Example: `assign out = data[2];`



```
module generate_set_of_MUX (a, b, f, sel);  
    input [0:3] a, b;  
    input sel;  
    output [0:3] f;  
    assign f = sel ? a : b;  
endmodule
```

Conditional operator
generates a MUX



- Point to note:
 - Whenever a conditional is encountered in the RHS of an expression, a 2-to-1 MUX is generated.
 - In the previous example, since the variables “a”, “b” and “f” are vectors, an array of 2-to-1 MUX-es are generated.
 - What hardware will be generated by the following?

```
assign f = (a==0) ? (c+d) : (c-d);
```



```
module generate_decoder (out, in, select);  
    input in;  
    input [0:1] select;  
    output [0:3] out;  
    assign out[select] = in;  
endmodule
```

Non-constant index in
expression on LHS
generates a decoder



- Point to note:
 - A constant index in the expression on the LHS will not generate a decoder.
 - Example: `assign out[5] = in;`
This will simply generate a wire connection.
 - As a rule of thumb, whenever the synthesis tool detects a variable index in the LHS, a decoder is generated.



```

module level_sensitive_latch (D, Q, En);
    input  D, En;
    output Q;
    assign Q = En ? D : Q;
endmodule

```

En	D	Q _n
0	x	Q _{n-1}
1	0	0
1	1	1

Generates a D-type latch

Here is an example to describe a sequential logic element using "assign" statement.



IIT KHARAGPUR




NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

11

- Modeling a simple S-R latch:

 

S	R	Q _n
1	1	Q _{n-1}
0	1	0
1	0	1
0	0	?



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

12

```

module sr_latch (Q, Qbar, S, R);
    input S, R;
    output Q, Qbar;

    assign Q = ~(R & Qbar);
    assign Qbar = ~(S & Q);
endmodule

module latchtest;
    reg S, R;    wire Q, Qbar;
    sr_latch LAT (Q, Qbar, S, R);
    initial
        begin
            $monitor ($time, "S=%b R=%b, Q=%b, Qbar=%b",
                    S, R, Q, Qbar);
            S = 1'b0; R = 1'b1;
            #5 S = 1'b1; R = 1'b1;
            #5 S = 1'b1; R = 1'b0;
            #5 S = 1'b1; R = 1'b1;
            #5 S = 1'b0; R = 1'b0;
            #5 S = 1'b1; R = 1'b1;
        end
endmodule

```



Simulation Output

```

0 S=0, R=1, Q=0, Qbar=1
5 S=1, R=1, Q=0, Qbar=1
10 S=1, R=0, Q=1, Qbar=0
15 S=1, R=1, Q=1, Qbar=0
20 S=0, R=0, Q=1, Qbar=1
and then the simulator hangs

```



END OF LECTURE 12



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

15



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 13: PROCEDURAL ASSIGNMENT

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

Behavioral Style: Procedural Assignment

- Two kinds of procedural blocks are supported in Verilog:
 - The “initial” block
 - Executed once at the beginning of simulation.
 - Used only in test benches; cannot be used in synthesis.
 - The “always” block
 - A continuous loop that never terminates
- The procedural block defines:
 - A region of code containing *sequential* statements.
 - The statements execute in the order they are written.



The “initial” Block

- All statements inside an “initial” statement constitute an “initial block”.
 - Grouped inside a “begin ... end” structure for multiple statements.
 - The statements starts at time 0, and execute only once.
 - If there are multiple “initial” blocks, all the blocks will start to execute concurrently at time 0.
- The “initial” block is typically used to write test benches for simulation:
 - Specifies the stimulus to be applied to the design-under-test (DUT).
 - Specifies how the DUT outputs are to be displayed / handled.
 - Specifies the file where the waveform information is to be dumped.



```

module testbench_example;
  reg a, b, cin, sum, cout;

  initial
    cin = 1'b0;

  initial
    begin
      #5 a = 1'b1; b=1'b1;
      #5 b = 1'b0;
    end

  initial
    #25 $finish;

endmodule

```

- The three “initial” blocks execute concurrently.
- The first block executes at time 0.
- The third block terminates simulation at time 25 units.



Some Short Cuts in Declarations

- “output” and “reg” can be declared together in the same statement.

`output reg [7:0] data;`
 instead of `output [7:0] data; reg [7:0] data;`

- A variable can be initialized when it is declared:

`reg clock = 0;`
 instead of `reg clock; initial clock = 0;`



The “always” Block

- All behavioral statements inside an “always” statement constitute an “always block”.
 - Multiple statements are grouped using “begin ... end”.
- An “always” statement starts at time 0 and executes the statements inside the block repeatedly, and never stops.
 - Used to model a block of activity that is repeated indefinitely in a digital circuit.
 - For example, a clock signal that is generated continuously.
 - We can specify delays for simulation; however, for real circuits, the clock generator will be active as long as there is power supply.



```

module generating_clock;
  output reg clk;

  initial
    clk = 1'b0; // initialized to 0 at time 0

  always
    #5 clk = ~clk; // Toggle after time 5 units

  initial
    #500 $finish;
endmodule

```

- “initial” and “always” blocks can coexist within the same Verilog module.
- They all execute concurrently; “initial” only once and “always” repeatedly.



- A module can contain any number of “always” blocks, all of which execute concurrently.
- The @(event_expression) part is required for both combinational and sequential circuit descriptions.

Basic syntax of “always” block:

```
always @(event_expression)
begin
    sequential_statement_1;
    sequential_statement_2;
    ...
    sequential_statement_n;
end
```



- Only “reg” type variable can be assigned within an “initial” or “always” block.
- Basic reason:
 - The sequential “always” block executes only when the event expression triggers.
 - At other times the block is doing nothing.
 - An object being assigned to must therefore remember the last value assigned (not continuously driven).
 - So, only “reg” type variables can be assigned within the “always” block.
 - Of course, any kind of variable may appear in the event expression (reg, wire, etc.).



Sequential Statements in Verilog

- In Verilog, one or more sequential statements can be present inside an “initial” or “always” block.
 - The statements are executed sequentially.
 - Multiple assignment statements inside a “begin ... end” block may either execute sequentially or concurrently depending upon the type of assignment.
 - Two types of assignment statements: blocking (`a = b + c;`) or non-blocking (`a <= b + c;`).
- The sequential statements are explained next.



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

25

(a) begin ... end

```
begin
  sequential_statement_1;
  sequential_statement_2;
  ...
  sequential_statement_n;
end
```

- A number of sequential statements can be grouped together using “begin .. end”.
- If n=1, “begin ... end” is not required.



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

26

(b) if ... else

```
if (<expression>)
    sequential_statement;
```

```
if (<expression>)
    sequential_statement;
else
    sequential_statement;
```

```
if (<expression1>)
    sequential_statement;
else if (<expression2>)
    sequential_statement;
else if (<expression3>)
    sequential_statement;
else default_statement;
```

- Each sequential_statement can be a single statement or a group of statements within "begin ... end".



(c) case

```
case (<expression>)
    expr1: sequential_statement;
    expr2: sequential_statement;
    ...
    exprn: sequential_statement;
    default: default_statement;
endcase
```

- Each sequential_statement can be a single statement or a group of statements within "begin ... end".
- Can replace a complex "if ... else" statement for multiway branching.
- The expression is compared to the alternatives (expr1, expr2, etc.) in the order they are written.
- If none of the alternatives matches, the default statement is executed.



- Two variations: “casez” and “casex”.
 - The “casez” statement treats all “z” values in the case alternatives or the case expression as don’t cares.
 - The “casex” statement treats all “x” and “z” values in the case item as don’t cares.

If state is “4'b01zx”, the second expression will give match, and next_state will be 1.

```
reg [3:0] state;  integer next_state;
casex (state)
  4'b1xxx : next_state = 0;
  4'bx1xx : next_state = 1;
  4'bxx1x : next_state = 2;
  4'bxxx1 : next_state = 3;
  default : next_state = 0;
endcase
```



END OF LECTURE 13





IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Lecture 14: PROCEDURAL ASSIGNMENT (CONTD.)

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

(d) “while” loop

```
while (<expression>)  
    sequential_statement;
```

- The “while” loop executes until the expression is *not true*.
- The sequential_statement can be a single statement or a group of statements within “begin ... end”.

Example:

```
integer mycount;  
initial  
begin  
    while (mycount <= 255)  
    begin  
        $display ("My count:%d", mycount);  
        mycount = mycount + 1;  
    end  
end
```



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

32

(e) “for” loop

```
for (expr1; expr2; expr3)
    sequential_statement;
```

- The “for” loop executes as long as the expression `expr2` is true.
- The `sequential_statement` can be a single statement or a group of statements within “begin ... end”.

- The “for” loop consists of three parts:
 - a) An initial condition (`expr1`).
 - b) A check to see if the terminating condition is true (`expr2`).
 - c) A procedural assignment to change the value of the control variable (`expr3`).
- The “for” loop can be conveniently used to initialize an array or memory.



Example:

```
integer mycount;
reg [100:1] data;
integer i;

initial
    for (mycount=0; mycount<=255; mycount=mycount+1)
        $display ("My count:%d", mycount);

initial
    for (i=1; i<=100; i=i+1)
        data[i] = 1'b0;
```



(f) “repeat” loop

```
repeat (<expression>)
    sequential_statement;
```

- The “repeat” construct executes the loop a fixed number of times.
- It cannot be used to loop on a general logical expression like “while”.

- The expression in the “repeat” construct can be a constant, a variable or a signal value.
 - If it is a variable or a signal value, it is evaluated only when the loop starts and not during execution of the loop.
- The sequential_statement can be a single statement or a group of statements within “begin ... end”.



Example:

```
reg clock;
initial
begin
    clock = 1'b0;
    repeat (100)
        #5 clock = ~clock;
end
```

Exactly 100 clock pulses
are generated.



(g) “forever” loop

```
forever
    sequential_statement;
```

- The “forever” loop is typically used along with timing specifier.
 - If delay is not specified, the simulator would execute this statement indefinitely without advancing \$time.
 - Rest of design will never be executed.

- The “forever” construct does not use any expression and executes forever until \$finish is encountered in the test bench.
 - Equivalent to a “while” loop for which the expression is always true.
- The sequential_statement can be a single statement or a group of statements within “begin ... end”.



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

37

```
// Clock generation using “forever” construct
reg clk;

initial
    begin
        clk = 1'b0;
        forever #5 clk = ~clk; // Clock period of 10 units
    end
```



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

38

Other Constructs Available

(time_value)

- Makes a block suspend for “time_value” units of time.
- The time unit can be specified using the ``timescale` command.

@ (event_expression)

- Makes a block suspend until “event_expression” triggers.
- Various keywords associated with “event_expression” shall be discussed with examples..



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

39

@ (event_expression)

- The event expression specifies the event that is required to resume execution of the procedural block.
- The event can be any one of the following:
 - a) Change of a signal value.
 - b) Positive or negative edge occurring on signal (*posedge* or *negedge*).
 - c) List of above-mentioned events, separated by “or” or comma.
- A “posedge” is any transition from {0, x, z} to 1, and from 0 to {z, x}.
- A “negedge” is any transition from {1, x, z} to 0, and from 1 to {z, x}.



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

40

- Examples:

- @ (in) // “in” changes
- @ (a or b or c) // any of “a”, “b”, “c” changes
- @ (a, b, c) // -- do --
- @ (posedge clk) // positive edge of “clk”
- @ (posedge clk or negedge reset) // positive edge of “clk” or negative edge of “reset”
- @ (*) // any variable changes



```
// D flip-flop with synchronous set and reset
module dff (q, qbar, d, set, reset, clk);
  input d, set, reset, clk;
  output reg q;    output qbar;

  assign qbar = ~q;

  always @ (posedge clk)
  begin
    if (reset == 0) q <= 0;
    else if (set == 0) q <= 1;
    else q <= d;
  end
endmodule
```



```
// D flip-flop with asynchronous set and reset
module dff (q, qbar, d, set, reset, clk);
  input d, set, reset, clk;
  output reg q;    output qbar;

  assign qbar = ~q;

  always @ (posedge clk or negedge set or negedge reset)
  begin
    if (reset == 0) q <= 0;
    else if (set == 0) q <= 1;
    else q <= d;
  end
endmodule
```



```
// Transparent latch with enable
module latch (q, qbar, din, enable);
  input din, enable;
  output reg q;    output qbar;

  assign qbar = ~q;

  always @ (din or enable)
  begin
    if (enable) q = din;
  end
endmodule
```



END OF LECTURE 14



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

45



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Lecture 15: PROCEDURAL ASSIGNMENT (EXAMPLES)

PROF. INDRANIL SENGUPTA
DEPARTMENT OF COMPUTER SCIENCE AND ENGINEERING

```
// A combinational logic example
module mux21 (in1, in0, s, f);
    input  in1, in0, s;
    output reg f;

    always @(in1 or in0 or s)
        if (s)
            f = in1;
        else
            f = in0;
endmodule
```

- The event expression in the “always” block triggers whenever at least one of “in1”, “in0” or “s” changes.
- The “or” keyword specifies the condition.



```
// A combinational logic example
module mux21 (in1, in0, s, f);
    input  in1, in0, s;
    output reg f;

    always @(in1, in0, s)
        if (s)
            f = in1;
        else
            f = in0;
endmodule
```

- An alternate way to specify the event condition by using comma instead of “or”.
- Supported in later versions of Verilog.




```
// A combinational logic example
module mux21 (in1, in0, s, f);
    input  in1, in0, s;
    output reg f;

    always @(*)
        if (s)
            f = in1;
        else
            f = in0;
endmodule
```

- An alternate way to specify the event condition by using a “*” instead of naming the variables.
- “*” is activated whenever *any* of the variables change.



```
// A sequential logic example
module dff_negedge (D, clock, Q, Qbar);
    input  D, clock;
    output reg Q, Qbar;

    always @(negedge clock)
        begin
            Q = D;
            Qbar = ~D;
        end
endmodule
```

- The keyword “negedge” means at the negative going edge of the specified signal.
- Similarly, we can use “posedge”.
- We can combine various triggering conditions by separating them by commas or “or”.



```
// 4-bit counter with asynchronous
reset
module counter (clk, rst, count);
    input clk, rst;
    output reg [3:0] count;
    always @(posedge clk or posedge rst)
        begin
            if (rst)
                count <= 0;
            else
                count <= count + 1;
        end
    endmodule
```

The event condition triggers when either a positive edge of "clk" comes, or a positive edge of "rst".



```
// Another sequential logic example
module incomp_state_spec (curr_state, flag);
    input [0:1] curr_state;
    output reg [0:1] flag;

    always @(curr_state)
        case (curr_state)
            0,1 : flag = 2;
            3   : flag = 0;
        endcase
    endmodule
```

The variable "flag" is not assigned a value in all the branches of the "case" statement.

- A latch (2-bit) will be generated for "flag".



```
// A small modification

module incomp_state_spec (curr_state, flag);
  input  [0:1] curr_state;
  output reg [0:1] flag;

  always @(curr_state)
  begin
    flag = 0;
    case (curr_state)
      0,1 : flag = 2;
      3    : flag = 0;
    endcase
  end
endmodule
```

Here the variable “flag” is defined for all the possible values of “curr_state”.

- A pure combinational circuit will be generated.
- The latch is avoided.



- When a “case” statement is incompletely decoded, the synthesis tool will infer the need for a latch to hold the residual output when the select bits take the unspecified values.
 - It is up to the designer to code the design in such a way that latch can be avoided where possible.



```
// A simple 4-function ALU
module ALU_4bit (f, a, b, op);
    input [1:0] op;      input [7:0] a, b;
    output reg [7:0] f;
    parameter ADD=2'b00, SUB=2'b01, MUL=2'b10, DIV=2'b11;

    always @(*)
        case (op)
            ADD : f = a + b;
            SUB : f = a - b;
            MUL : f = a * b;
            DIV : f = a / b;
        endcase
endmodule
```



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

55

```
module priority_encoder (in, code);
    input [7:0] in;
    output reg [2:0] code;
    always @(in)
        begin
            if (in[0]) code = 3'b000;
            else if (in[1]) code = 3'b001;
            else if (in[2]) code = 3'b010;
            else if (in[3]) code = 3'b011;
            else if (in[4]) code = 3'b100;
            else if (in[5]) code = 3'b101;
            else if (in[6]) code = 3'b110;
            else if (in[7]) code = 3'b111;
            else
                code = 3'bxxx;
        end
endmodule
```

- The inputs bits are checked sequentially one by one (in order of priority).
 - “in[0]” has the highest priority.
 - For simultaneously active inputs, the first active input encountered will be encoded.



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES


Hardware Modeling Using Verilog

56

```

module bcd_to_7seg (bcd, seg);
  input [3:0] bcd;
  output reg [6:0] seg;
  always @(bcd)
    case
      0: seg = 6'b0000001;
      1: seg = 6'b1001111;
      2: seg = 6'b0010010;
      3: seg = 6'b0000110;
      4: seg = 6'b1001100;
      5: seg = 6'b0100100;
      6: seg = 6'b0100000;
      7: seg = 6'b0001111;
      8: seg = 6'b0000000;
      9: seg = 6'b0000100;
      default : seg = 6'b1111111;
    endcase
endmodule

```

 

Segment bit assignment:
(a, b, c, d, e, f, g)

A segment glows when the corresponding bit of seg is 0.



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

57

```

// An n-bit comparator
module compare (A, B, lt, gt, eq);
  parameter word_size = 16;
  input [word_size-1:0] A, B;
  output reg lt, gt, eq;

  always @ (*)
    begin
      gt = 0; lt = 0; eq = 0;
      if (A > B) gt = 1;
      else if (A < B) lt = 1;
      else eq = 1;
    end
endmodule

```

For actual synthesis, it is common to have a structured design representation of the comparator.



IIT KHARAGPUR

NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

58

```
// A 2-bit comparator
module compare (A1, A0, B1, B0, lt, gt, eq);
  input  A1, A0, B1, B0;
  output reg  lt, gt, eq;

  always @ (A1, A0, B1, B0)
    begin
      lt = ({A1,A0} < {B1,B0});
      gt = ({A1,A0} > {B1,B0});
      eq = ({A1,A0} == {B1,B0});
    end
endmodule
```



```
module alu_example (alu_out, A, B, operation, en);
  input [2:0] operation; input [7:0] A, B;
  input en;
  output [7:0] alu_out; reg [7:0] alu_reg;

  assign alu_out = (en == 1) ? alu_reg : 4'bz;
  always @ (*)
    case (operation)
      3'b000 : alu_reg = A + B;
      3'b001 : alu_reg = A - B;
      3'b011 : alu_reg = ~ A;
      default : alu_reg = 4'b0;
    endcase
endmodule
```



END OF LECTURE 15



IIT KHARAGPUR



NPTEL ONLINE
CERTIFICATION COURSES

Hardware Modeling Using Verilog

61